



FACULTY OF ENGINEERING

CAIRO UNIVERSITY

LAB 2

INTRODUCTION TO VHDL

CMPS301: COMPUTER ARCHITECTURE COURSE

EXERTEED FROM DR. ADNAN SHAOUT- *THE UNIVERSITY OF MICHIGAN-DEARBORN*



What we learned last time

- How to create Entity

- How to implement Architecture

- What different modeling could be used (Dataflow , behavioral, structural)

- Code is Concurrent not sequential

- “WHEN ... ELSE” statement is concurrent only

- Signals are wires

- Different data types

- How to reuse previously created entity (component instantiation a.k.a port mapping)



Objectives

- Review Conditional Concurrent statements
- Others Keyword
- Learn about Generic entities
- Learn about For-Generate and if-Generate

Remember Mux4x1

ENTITY mux **IS**


PORT(in0,in1,in2,in3: IN std_logic;

sel : IN std_logic_vector (1 DOWNTO 0);

out1: OUT std_logic);

END mux4;

Intro to VHDL

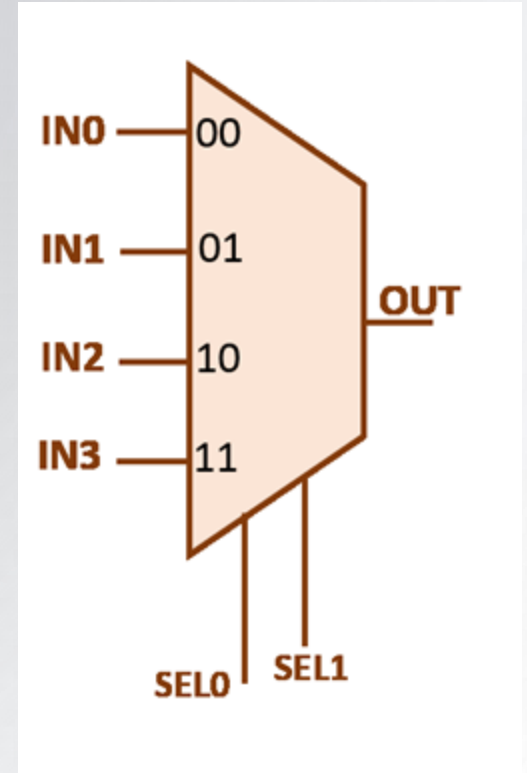

When ... ELSE / With ... Sel

```
ARCHITECTURE a_mux OF mux  
BEGIN
```

```
    out1 <=    in0 WHEN sel = "00"  
      ELSE in1 WHEN  sel = "01"  
      ELSE in2 WHEN  sel = "10"  
      ELSE in3;
```

```
END a_mux;
```



```
ARCHITECTURE b_mux OF mux  
BEGIN
```

```
  with sel select
```

```
  out1 <=  
    in0 when "00",  
    in1 when "01",  
    in2 when "10",  
    in3 when "11";
```

```
END b_mux;
```

When ... ELSE / With ... Sel

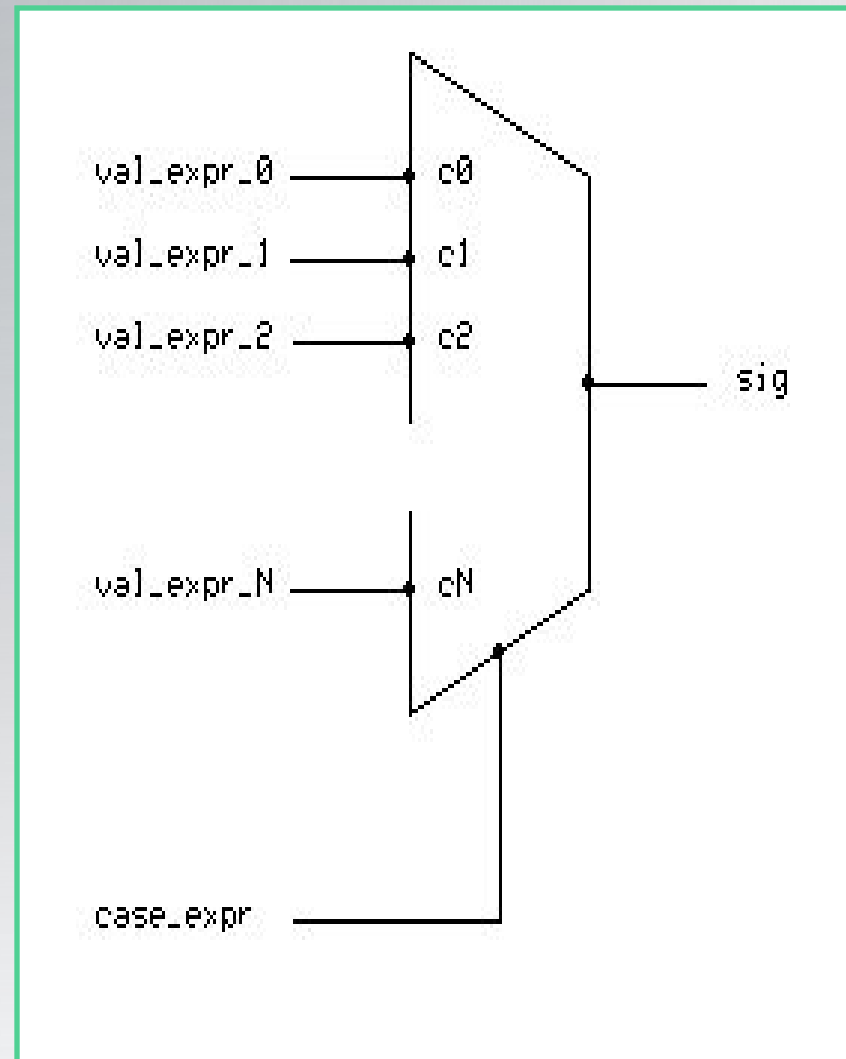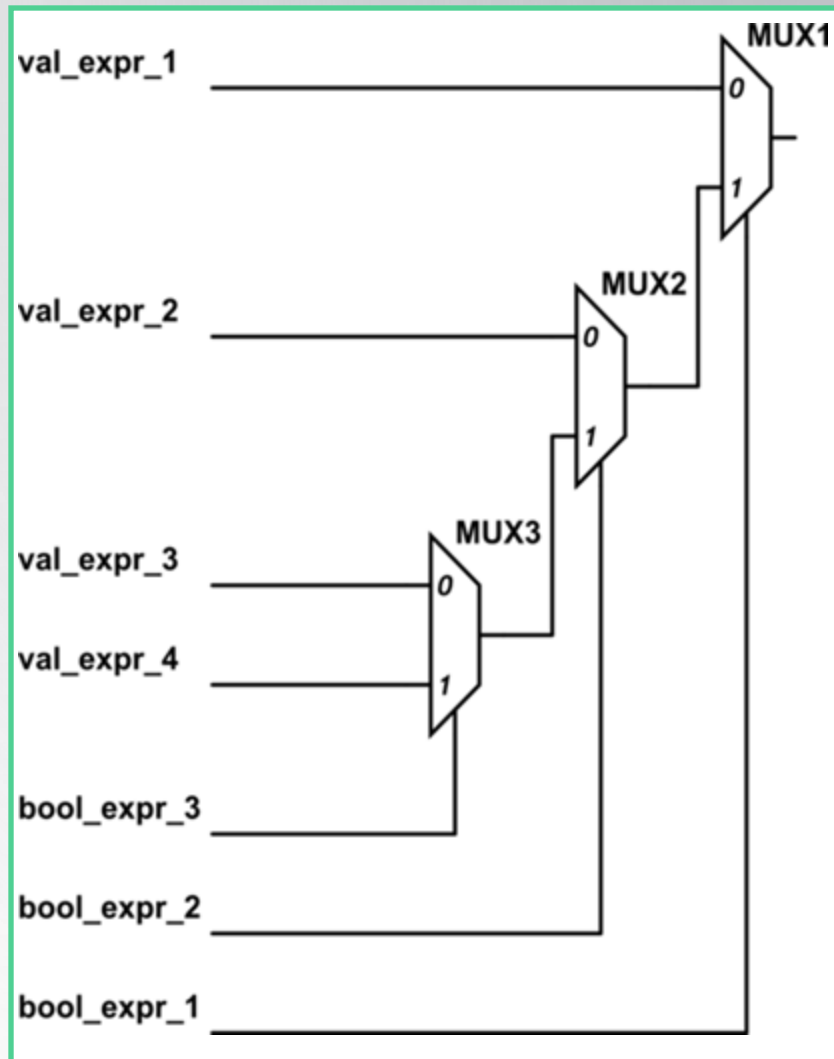

When ... ELSE / With ... Sel

What happens if we missed a case ?!


```
F <= a when Sel = "00";  
-- what is the Value of F if Sel is not 00 ?!!!!
```

When ... ELSE / With ... Sel

What happens if we missed a case ?!

```
F <= a when Sel = "00";  
-- what is the Value of F if Sel is not 00 ?!!!!
```

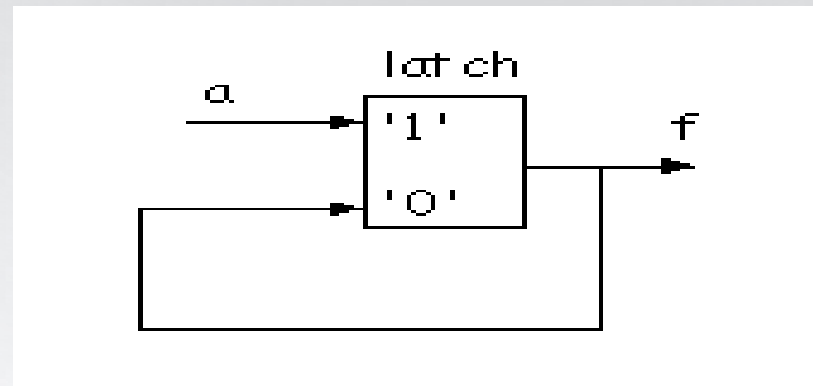A latch will be formed to save previous value





Objectives

- Review Conditional Concurrent statements

- Others Keyword

- Learn about Generic entities

- Learn about For-Generate and if-Generate

A decorative graphic consisting of several vertical and diagonal lines of varying lengths, some ending in small circles, resembling a stylized circuit board or a network diagram. The lines are black and the circles are white with black outlines.

A decorative graphic consisting of several vertical and diagonal lines of varying lengths, some ending in small circles, resembling a stylized circuit board or a network diagram. The lines are black and the circles are white with black outlines.

A decorative graphic consisting of several vertical and diagonal lines of varying lengths, some ending in small circles, resembling a stylized circuit board or a network diagram. The lines are black and the circles are white with black outlines.

```
F <= "000000000000000000000000000000000000";  
F <= x"00000000";      -- hexadecimal  
F<= (Others => '0');
```

-
- A decorative graphic consisting of several vertical and diagonal lines of varying lengths, some ending in small circles, resembling a stylized circuit board or a network diagram. The lines are black and the circles are white with black outlines.

“OTHERS” Keyword

Use “OTHERS” Whenever you want to:

- Set a bus to several zeros or several 1s but you don't want to write it.
- Set a certain bit to value and others zero
- Generic Case in Switch Cases

Example

```
With S select  
F <= a when "0010",  
      b when others;
```



Objectives


- Review Conditional Concurrent statements

- Others Keyword

- Learn about Generic entities

- Learn about For-Generate and if-Generate



Let's build a full adder 😊

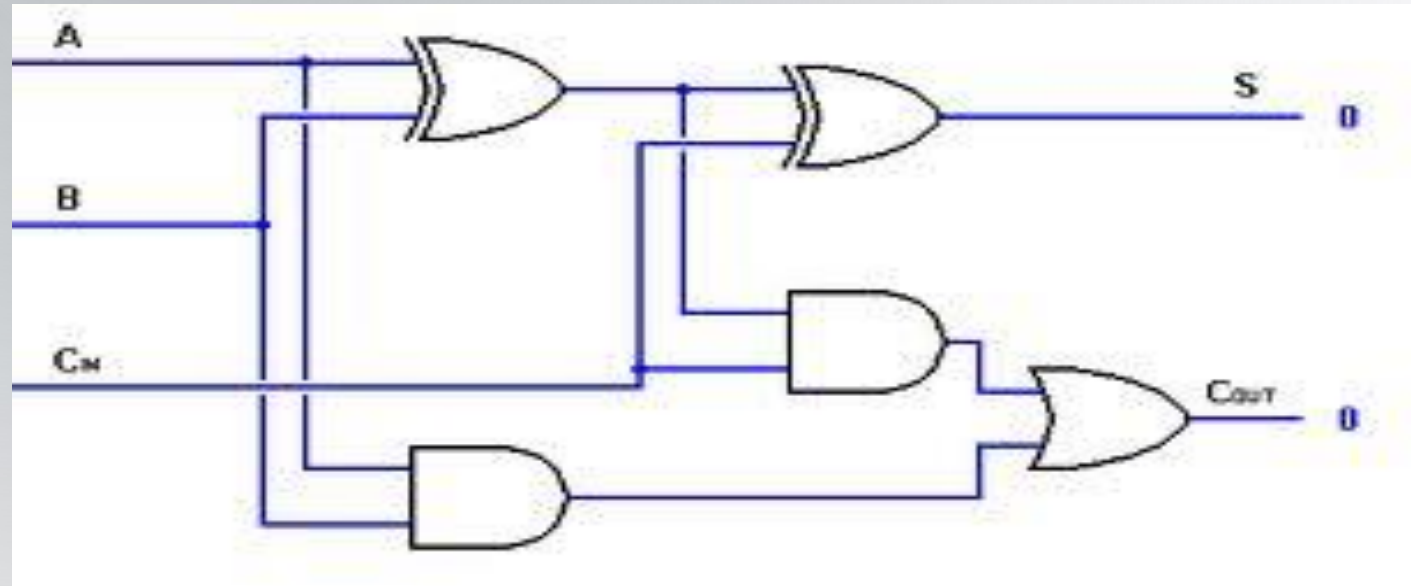

1bit-adder example


```
ENTITY my_adder IS    -- single bit adder
    PORT( a,b,cin : IN std_logic;
          s,cout : OUT std_logic);
END my_adder;

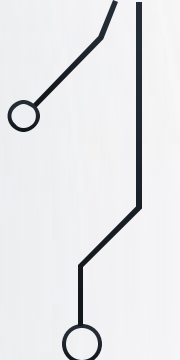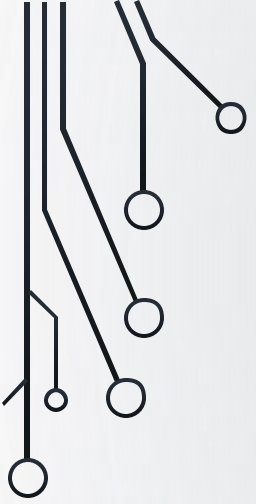ARCHITECTURE a_my_adder OF my_adder IS
BEGIN
    s <= a XOR b XOR cin;
    cout <= (a AND b) or (cin AND (a XOR b));
END a_my_adder;
```



Now how to build 4-bits full adder from 1-bit full adder?

Carry-Propagate Adder

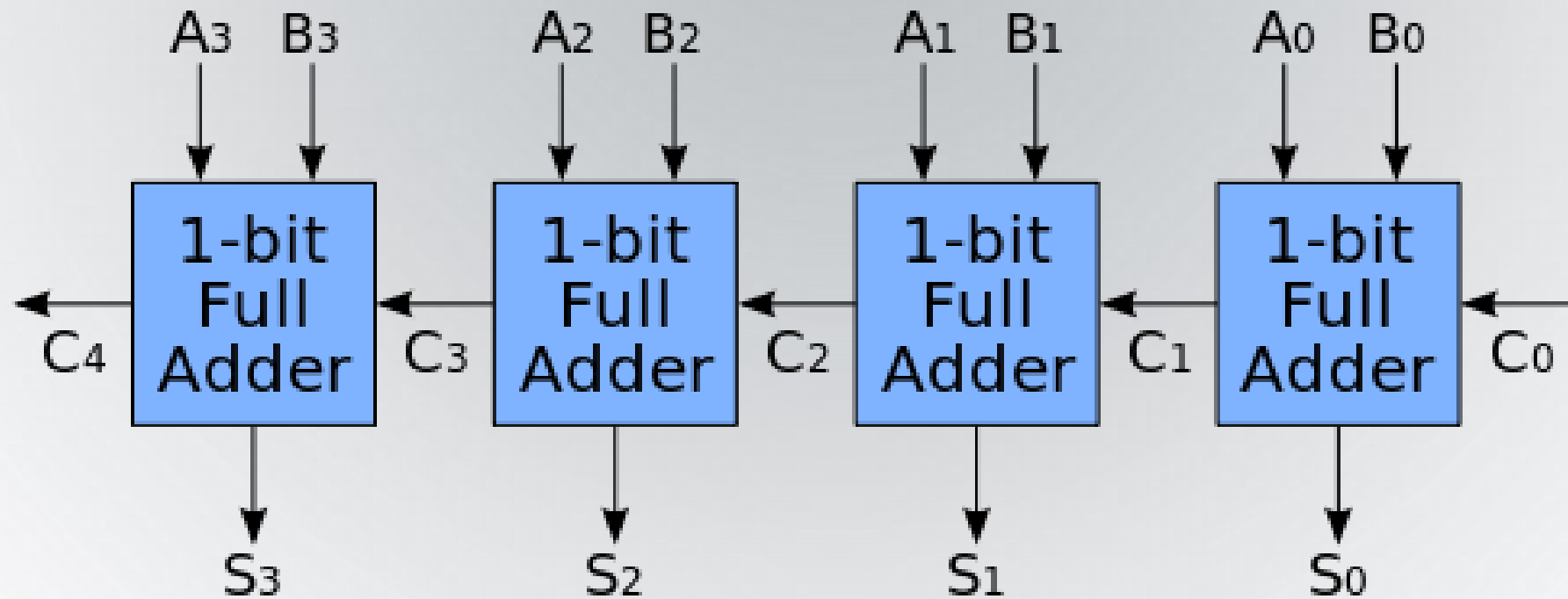

4 Bit-full Adder

ENTITY my_nadder **IS**

PORT (a, b : IN std_logic_vector(3 DOWNT0 0) ;
cin : IN std_logic;
s : OUT std_logic_vector(3 DOWNT0 0);
cout : OUT std_logic);

END my_nadder;

ARCHITECTURE a_my_nadder **OF** my_nadder **IS**

COMPONENT my_adder **IS**

PORT(a,b,cin : **IN** std_logic; s,cout : **OUT** std_logic);

END COMPONENT;

SIGNAL temp : std_logic_vector(4 **DOWNTO** 0);

BEGIN

Temp(0) <= cin;

f0: my_adder **PORT MAP**(a(0),b(0),temp(0),s(0),temp(1));

f1: my_adder **PORT MAP**(a(1),b(1),temp(1),s(1),temp(2));

f2: my_adder **PORT MAP**(a(2),b(2), temp(2),s(2),temp(3));

f3: my_adder **PORT MAP**(a(3),b(3), temp(3),s(3),temp(4));

Cout <= temp(4);

END a_my_nadder;

From Specific to Generic entities

```
ENTITY my_nadder IS
```

```
PORT (a, b : IN std_logic_vector(3 DOWNT0 0) ;  
        cin : IN std_logic;  
        s : OUT std_logic_vector(3 DOWNT0 0);  
        cout : OUT std_logic);
```

```
END my_nadder;
```

Now how can we change 8-bits
full adder to generic n-bit full adder?

From Specific to Generic entities

ENTITY my_nadder **IS**

PORT (a, b : IN std_logic_vector(n-1 DOWNT0 0) ;
cin : IN std_logic;
s : OUT std_logic_vector(n-1 DOWNT0 0);
cout : OUT std_logic);

END my_nadder;

Notice the use of 'n' here
But where did we define "n"

Integer another data type

From Specific to Generic entities

```
ENTITY my_nadder IS  
GENERIC (n : integer := 8);  
PORT (a, b : IN std_logic_vector(n-1 DOWNT0 0) ;  
        cin : IN std_logic;  
        s : OUT std_logic_vector(n-1 DOWNT0 0);  
        cout : OUT std_logic);  
  
END my_nadder;
```

Add generic
input

8 is default value and
could be override
while instantiation

Notice the use of 'n' here
But where did we define "n"

ARCHITECTURE a_my_nadder **OF** my_nadder **IS**

COMPONENT my_adder **IS**

PORT(a,b,cin : **IN** std_logic; s,cout : **OUT** std_logic);

END COMPONENT;

SIGNAL temp : std_logic_vector(4 **DOWNTO** 0);

BEGIN

temp(0) <= cin;

f0: my_adder **PORT MAP**(a(0),b(0),temp(0),s(0),temp(1));

f1: my_adder **PORT MAP**(a(1),b(1),temp(1),s(1),temp(2));

f2: my_adder **PORT MAP**(a(2),b(2), temp(2),s(2),temp(3));

f3: my_adder **PORT MAP**(a(3),b(3), temp(3),s(3),temp(4));

Cout <= temp(4);

END a_my_nadder;

ARCHITECTURE a_my_nadder **OF** my_nadder **IS**

COMPONENT my_adder **IS**

PORT(a,b,cin : **IN** std_logic; s,cout : **OUT** std_logic);

END COMPONENT;

SIGNAL temp : std_logic_vector(**n** **DOWNTO** 0);

Change size
of signal

BEGIN

temp(0) <= cin;

f0: my_adder **PORT MAP**(a(0),b(0),temp(0),s(0),temp(1));

f1: my_adder **PORT MAP**(a(1),b(1),temp(1),s(1),temp(2));

f2: my_adder **PORT MAP**(a(2),b(2), temp(2),s(2),temp(3));

f3: my_adder **PORT MAP**(a(3),b(3), temp(3),s(3),temp(4));

Cout <= temp(4);

END a_my_nadder;

ARCHITECTURE a_my_nadder **OF** my_nadder **IS**

COMPONENT my_adder **IS**

PORT(a,b,cin : **IN** std_logic; s,cout : **OUT** std_logic);

END COMPONENT;

SIGNAL temp : std_logic_vector(**n** **DOWNTO** 0);

Change size
of signal

BEGIN

temp(0) <= cin;

loop1: **FOR** i **IN** 0 **TO** n-1 **GENERATE**

fx: my_adder **PORT MAP**(a(i),b(i),temp(i),s(i),temp(i+1));

i → is not visible outside the for generate

END GENERATE;

Cout <= temp(n);

END a_my_nadder;

For....Generate

We use it when we want to generate more than one component of the same type

↙ i → is not visible outside the for generate

```
loop1: FOR i IN 0 TO n-1 GENERATE
```

```
    fx: my_adder PORT MAP(a(i),b(i),temp(i-1),s(i),temp(i));
```

```
END GENERATE;
```

The (for ...generate) is not a Software Sequential loop .. It is like writing this line n times and they execute **concurrently. Generates N hardware**

Genericcont.

So after I made my entity generic when I instantiate I do the following

u0: my_nadder **GENERIC MAP (16)** PORT MAP (.....)

I indicate here the value of the generic data

Generic could be more than one parameter like generic
(n,m : integer;)
Even could be with different type

Genericcont.

In simulation

```
vsim my_nadder -g<genericName>=<value>
```

Example

```
vsim my_nadder -gn=8
```

Common Errors

During Coding:

- Mix the use of bit & std_logic
- Using port map inside a condition
- Size of Input Vector not Equal Size of Output Vector

During Simulation:

- Simulating without compiling last changes
- Not forcing all input ports at initialization
- Force values on output port/signal



Summary

- Review on (When .. Else / With...Sel)

- Use of “OTHERS” keyword

- Make Generic Entities & use them

- Use “for ... Generate”

- Check for “if..Generate”